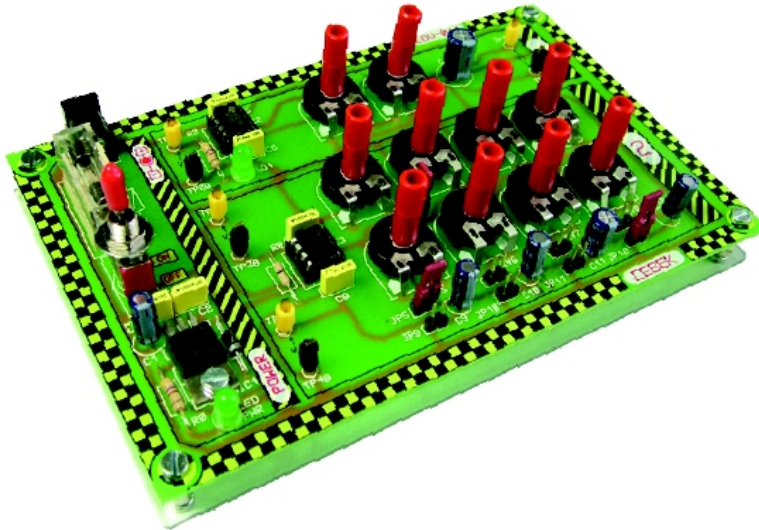


**EDU-014. Astable Ne555**



EDU-014

The EDU is a mini composed by two NE in astable configuration with the necessary components to experiment without external elements the different variables and concepts indicated in the documentation and the practices. The EDU exhibits the operating mode and answer of a free oscillation multivibrator based on the “ ”. Experimenting through the practices the description of its internal structure operating answer and characteristics of its astable configuration Impulse width operating time frequency operating cycle charge and discharge graphics configuration of external components and output answer

**Practice** Description of the astable NE Capacitor charge and discharge PCS and PCI switching levels Observation output wave forms and the capacitor

**Practice** Timing Importance of the resistor value in the impulse width and the period

**Practice** Resolution of Capacitor and R and R values according the required impulse width period and frequency

**EDU-014. Astable NE555**

**Warranty and Do not forget.**

Cebek educational modules included in the EDU serial offer several practices to analyse, experiment and to learn basic knowledge on the studied theme. Nevertheless, their function is not to make a mini-class on each theme, but to complete and to be used as basis, as well as to allow to experiment on the theoretical theme evocated by the teacher. For this reason, we suggest you to use modules form the EDU serial under the supervision and the direction of a teacher.

Cebek doesn't offer a consulting service as concern the theoretical or the operating principles concerning the theme deal with the module. It only offers a technical assistance regarding questions and problems coming from the circuit's internal operating mode.


All Cebek modules included in the EDU serial have a warranty of 3 years as concerning components and labour man. All damages provoked by external causes (from the circuit), as well as wrong connections or installations or due to an operating mode no indicated into the module's documentation won't be covered by the warranty. More over, all wrong or incorrect handling won't be excluded from the warranty. For any claim, you have to present the corresponding invoice.

To contact our technical department, you can send a message to [sat@cebek.com](mailto:sat@cebek.com), or a fax :Nº+34.93.432.29.95 or a mail to the following address: CEBEK, c/Quetzal, 17-21, 08014 Barcelona (SPAIN).

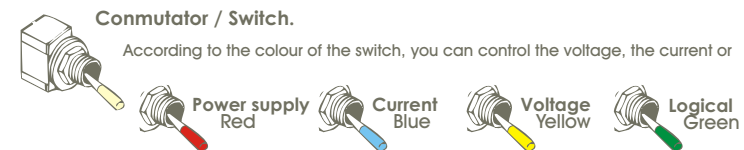**Rules and Identification of the EDU serial elements.**

To make easier the identification and for a single rule as concern different practices and educational Cebek modules, all common elements will answer to colour code and to a shape.

**Test Point. (TP).**  
It allows to connect oscilloscope's or multimeter extremities to read parameters relating to the practice. According to its colour, it will indicate that the Test Point (TP) is connected to the positive or to the negative of the circuit, as well as reads concerning current, voltage, load, etc....



EDU-014

## EDU-014. Astable NE555

### Before to start...

Before to start a practice, Before to start a practice, it is very important to carefully read its instructions manual as well as corresponding indications.

You have to correctly make connections concerning indicated contact points, otherwise measures depending on these connections will be confuses or incorrects.

Do not make any connection or short-circuits no specified in this manual, to avoid to damage the module.

If the illumination Led indicated as "PWR" doesn't light on or if its function is suddenly stopped, you have to immediately disconnect the devise from the power supply and to check if there is no short-circuit as well as the fuse state.

Even if you can make this practice following instructions described into this manual, we suggest you to make this practice under the supervision of a teacher allowing to consult, to increase or to help regarding concepts described herewith.


On the circuit, each practice will be delimited by a rectangle with the corresponding number. One or several experiments could be reported to this practice.

### Module's power supply.

The module is supplied at 12 V DC. You have to use a laboratory stabilised power supply like our Cebek FE-113. The circuit's feeding is done through the male connector inserted on the board, do not inject signal on any other terminal placed on the circuit. Once supplied, the circuit offers necessaries voltages to make experiments with each practice. To connect the power supply, the module includes a cable with a male connector at one extremity and wires at the other extremity.

Respecting the connector polarity, you have to connect each terminal to the corresponding and respective terminal of the power supply. Then, you could insert it on the module.

Note: The circuit fuse is 250mA.

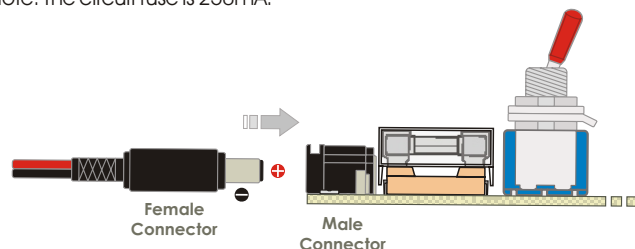

### Required Material.

You won't need any additional material or components to experiment with this module. You only need basis measure instruments to obtain and to compare obtained values from this practice. For this module, you will need one or several multimeters with their voltmeter, ammeter or ohmmeter functions. If you have an oscilloscope, you could also use it to substitute the voltmeter.

### Bibliography.

- With Google: NE555
- With Google: Ne555 Fairchild
- Electronics Principles, (Mc Graw Hill)

## EDU-014. Astable NE555

### The " "

The " " maintains today several characteristics that make it ideal in innumerable applications mainly as accurate timer

Distributed by different manufacturers according to its origin it is denominated NE LM CA MC etc It is also available the version which encapsulates in a same integrated two NE the NE

Among its characteristics it emphasizes its high accuracy which it can reach as timer even if it is submitted to voltage and temperature variations It can be supplied with voltages between and V DC and its stability in frequency by each Celsius degree os of More over it requires the use of few external components and it can supply a maximum output current up to mA




### NE 555's pins




The NE can mainly operate in two different configurations as monostable multivibrator or as astable multivibrator



### Monoestable 555

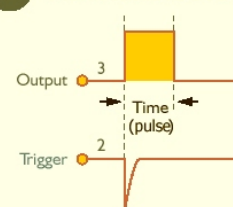

### Astable 555

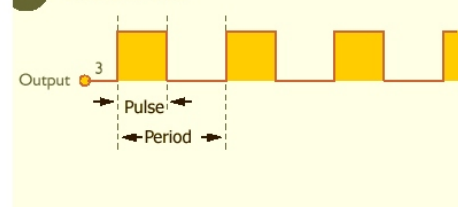

In Astable mode it generates a constant square signal composed by a impulse at high level followed by another one at low level where the width of the pulse at high level can be adjusted as well as the part of the cycle at low level

In Monoestable mode the NE produces a single accurate impulse which can be established from microseconds up to hours



### Practice Practice s Internal structure and description

The drawing of the NE s internal structure also shows that through the connection of the two external resistors R and R and the C capacitor connections to configure the in astable mode

Internally the NE is basically structured by a voltage division with three resistors of the same value two comparators a RS flip flop a NPN and a Reset

The three internal resistors constitute two levels that determine the switching points on the comparators the superior PCS Vdc and the inferior PCI Vdc



**Exercise Operating cycle and configuration resistors**

The capacitor's charge constant is determined by R and R being equal to R R C. The discharge is done through R for this reason the constant is R C.

As both time constants are different according to the R and R value the operating cycle will be established between and

See now the R R and C translation to the practice. Corresponding FQ FQ and C. The two resistors are in this case variables allowing of establish different oscillation frequencies.

When FQ is superior to FQ the operating cycle is nearing to and the LED blinks at a lower speed with a light on and light off cycle very similar.

At the opposite if FQ is superior to FQ the operating cycle is practically equal to and the LED is almost completely fixe with a short blinking few perceptible.


Note In order to check this PQ point do not completely place it at the minimum but leave it in a lower possible value.

The minimum and maximum in both resistors is different from one to the other. The objective of the exercise is to identify in which position left or right have been placed each one considering the influence of both resistors in the result of the operating cycle and oscillation of the LED.

**Practice Impulse width period and frequency**



Electrical drawing - Practice 2

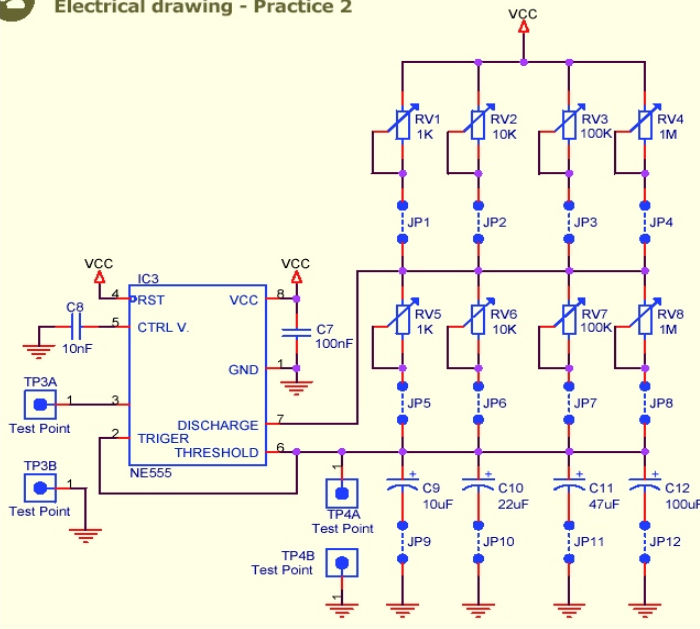

**Practice Impulse width period and frequency Part II**  
From charge and discharge constants it can be determined formulas to calculate the impulse width the period and consequently the frequency and the operating cycle.

**Formula to calculate Astable NE**

	W	T	second	f	Hertz	D	R	R	en ohms	C	en Farades
Impulse width	W	W					R	R			
Period	T	T					R	R	C		
Frequency	f	f					R	R	C		invert regarding period one
Operating cycle	D	D					R	R	R	R	Impulse width Period

**Practice** allows to configure different combinations from "R" "R" and "C" through the closure of the corresponding jumpers and with the consistent impulse period and frequency difference.

R can be RV RV RV or RV closing the corresponding JP JP JP or JP jumpers.

R is selectable between RV RV RV and RV through the closing of one of JP JP JP and JP jumpers.

C will obtain the C C C or C value according to the corresponding closure of JP JP JP or JP jumpers.

For instance for a KR a KR and a uF capacitor you have to close JP JP and JP. And it is the same thing RV RV and C will be selected.

The exercise will consist in writing in each square the combination of jumpers which would configure necessary R R and capacitor to obtain the indicated value as well as the operating cycle monitoring through the oscilloscope.

Practice 2.

	JP1	JP6	JP11
W = 358,28 mseg.			
f = 2,55 Hz.			
T = 145,53 seg.			
W = 76,23 seg.			
f = 1,45 Hz.			
T = 4,57 seg.			